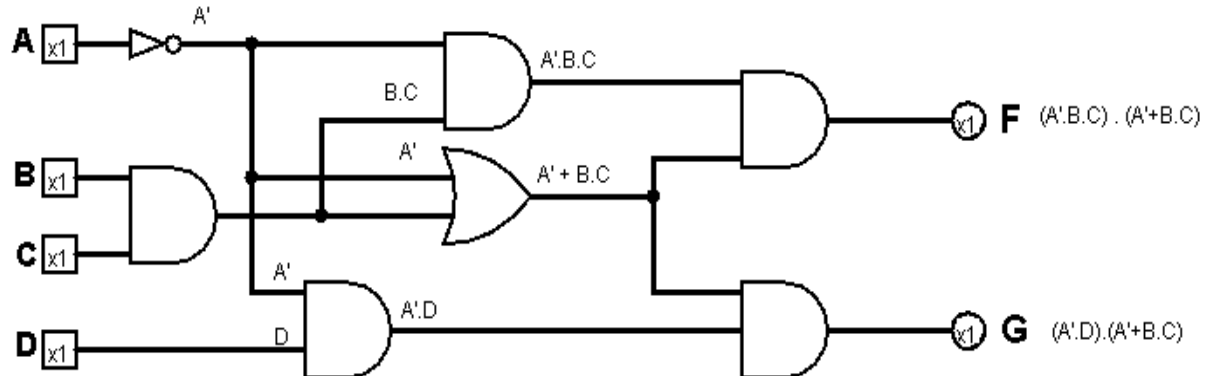




Lab #1 (MODEL ANSWER)

Q1: (5 points) Obtain the simplified Boolean expressions for output F and G in terms of the input variables in the circuit of the following figure:



Using Boolean algebra:

$$\begin{aligned} F &= (\bar{A}.B.C).(\bar{A} + B.C) \\ &= \bar{A}BC\bar{A} + \bar{A}BCBC \\ &= \bar{A}BC + \bar{A}BC \\ &= BC.(\bar{A} + \bar{A}) \\ &= B.C.\bar{A} \end{aligned}$$

$$\begin{aligned} G &= (\bar{A}.D).(\bar{A} + B.C) \\ &= \bar{A}D\bar{A} + \bar{A}DBC \\ &= \bar{A}D + \bar{A}DBC \\ &= \bar{A}D.(1 + BC) \\ &= \bar{A}D \end{aligned}$$

Q1: (5 points) Draw the logic circuits for the simplified Boolean expression from Q1 using Logisim software.

